



6. Analog Sensors

The next sketch & electronics diagram demonstrates analog input by reading an analog sensor as a potentiometer (or trimpot) on analog pin 0 and turning on and off a LED connected to digital pin 2. The amount of time the LED will be on and off depends on the value obtained by `analogRead()`.

Circuit

- potentiometer: center pin of the potentiometer to the analog input 0, one side pin (either one) to ground, the other side pin to +5V
- LED: a 220Ω resistor bridges digital output 2 to the anode (long leg) of the LED, the cathode (short leg) attached to ground.

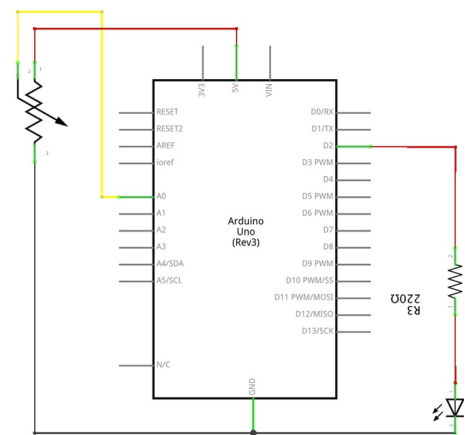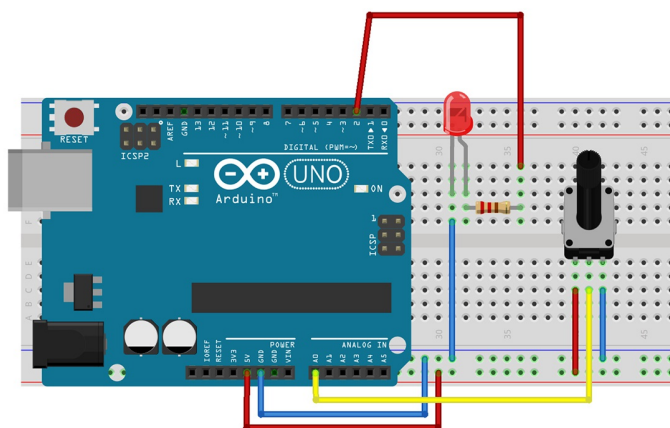Actually the resistor can also go in between the cathode and ground as in a series circuit the order of components does not matter as the current has to pass through all the parts!



Code

```
int sensorPin = A0;    // select the input pin for the potentiometer
int ledPin = 2;        // select the pin for the LED
int sensorValue = 0;    // variable to store the value coming from the sensor

void setup() {
    // declare the ledPin as an OUTPUT
    pinMode(ledPin, OUTPUT);
    // there is no need to set our analog in pin
}

void loop() {
    // read the value from the sensor:
    sensorValue = analogRead(sensorPin);
    // turn the ledPin on
```

```
digitalWrite(ledPin, HIGH);  
// stop the program for <sensorValue> milliseconds:  
delay(sensorValue);  
// turn the ledPin off:  
digitalWrite(ledPin, LOW);  
// stop the program for for <sensorValue> milliseconds:  
delay(sensorValue);  
}
```